

**Q11: The following serial data are applied to the flip-flop through the AND gates as indicated in Figure 11. Determine the resulting serial data that appear on the Q output. There is one clock pulse for each bit time. Assume that Q is initially 0 and that PRE and CLR are HIGH. Rightmost bits are applied first.**

$J_1: 1010011$

$J_2: 0111010$

$J_3: 1111000$

$K_1: 0001110$

$K_2: 1101100$

$K_3: 1010101$



 


Figure (11)

 **Q12:** For the circuit in Figure 12(a), complete the timing diagram in Figure 12(b) by showing the Q output (which is initially LOW). Assume PRE and CLR remain HIGH.



**(a)**

 

(b)